



RADIO MODS DATABASE



Power supply for 3 to 30 Volts 2,5 A


This is a project for anyone that knows something about electronics.

The power supply is versatile and stable with variable tensions and protected with power sort.

This project solves most of the problems in any electronic jobs.

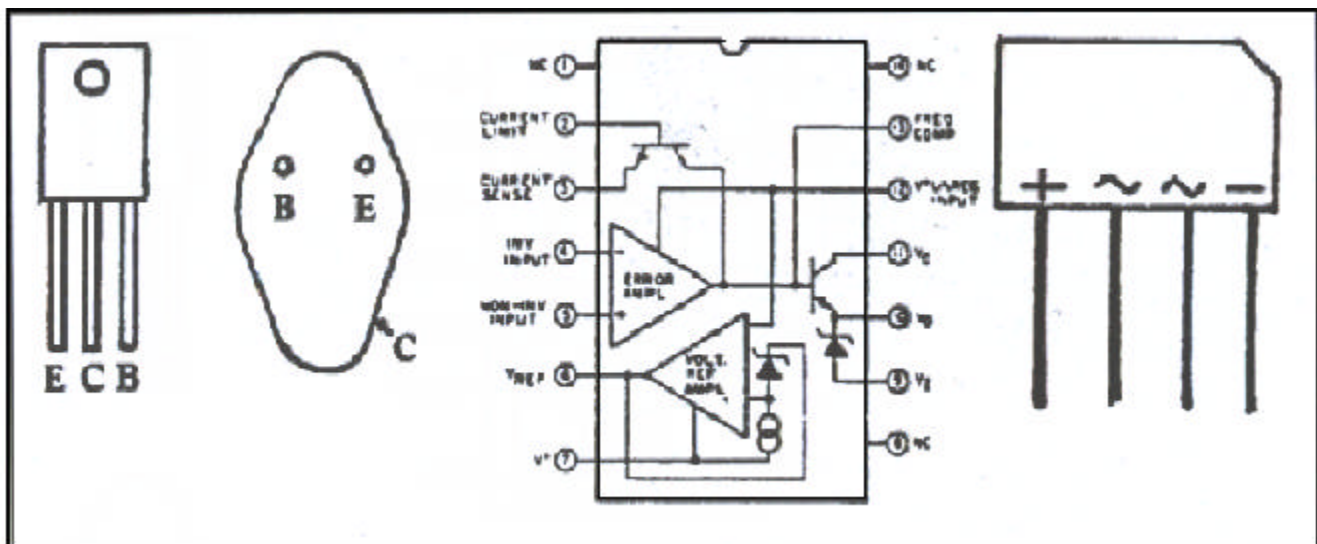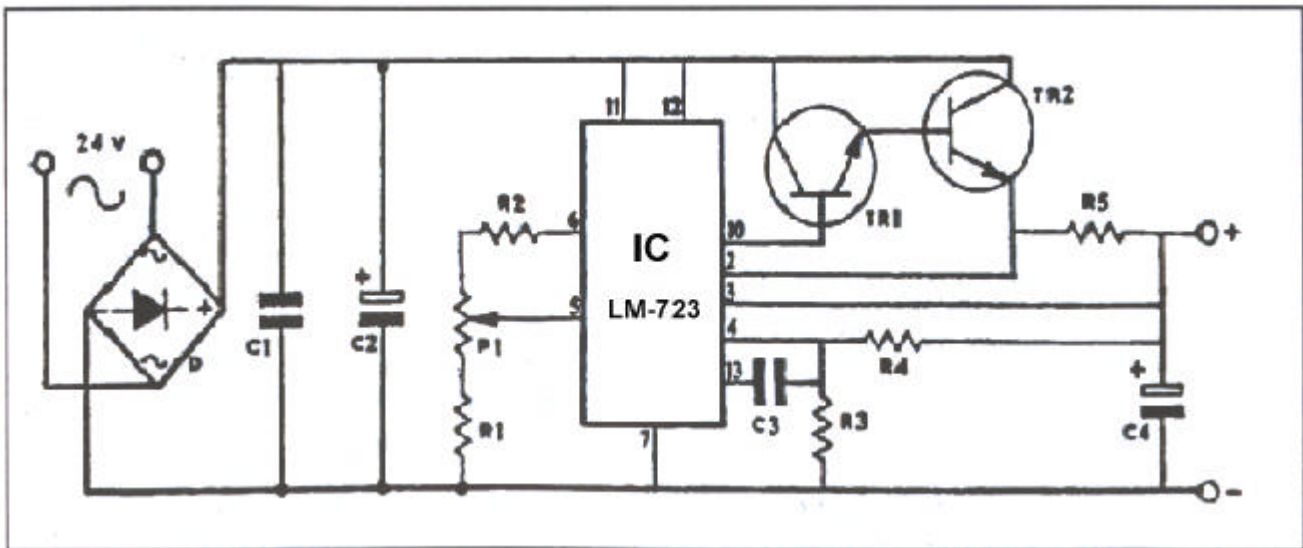The circuit has stable tensions and works with IC - LM-723 which can be adjusted for any tension varying between 2 and 37V DC



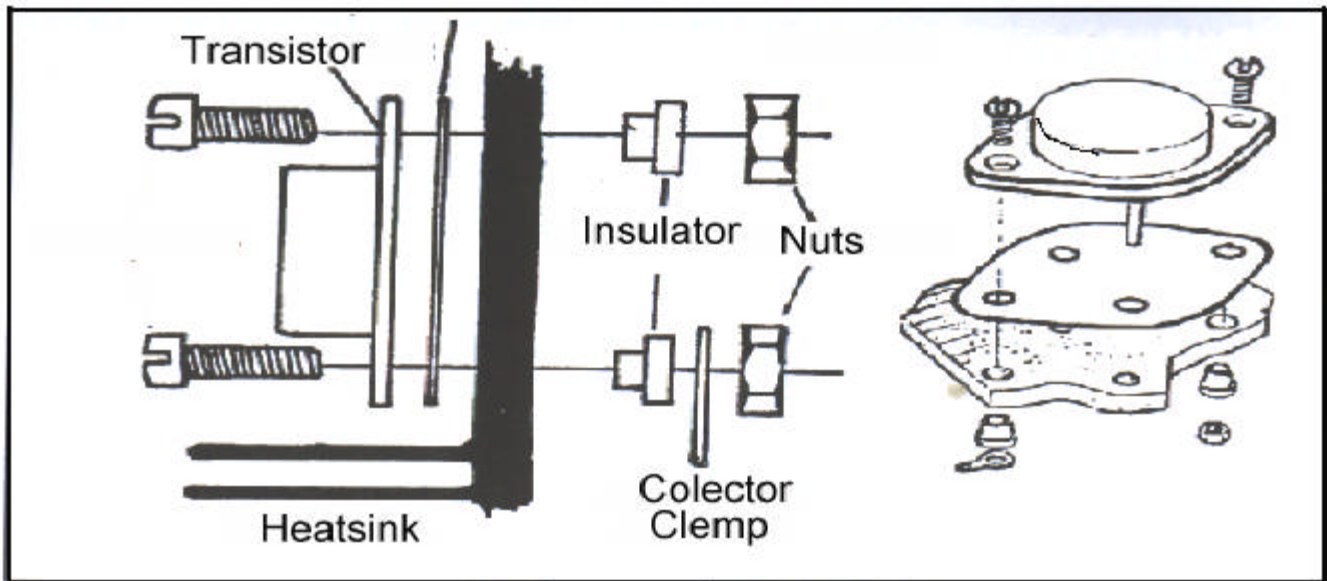

R1	562Ω 1/2W
R2	1,2KΩ 1/2W
R3	3,9KΩ 1/2W
R4	15KΩ 1/2W
R5	0,15Ω 1W
P1	10KΩ
C1	100nF
C2	2200uF/35-40V
C3	100pF
C4	100uF/35V
D	3A
IC	LM723
TR1	BD135
TR2	2N3055